

Introduction to HDL

Name: Santos – Canoneo - Villamor Date: **10/10/23**

Due Date: **10/14/23**

Lab Exercise 1 : Labex
VHDL Code and Simulation

Laboratory Exercise1:


Given the logic equation $Y = AB' + C'$ implement this equation using two inverters, one OR gate and one AND under the Quartus 2 environment.
Upon completion of the schematic entry portion of the example, simulate the circuit and print out copies of the circuit & simulation results.

Draw a Logic Diagram and Truth Table (in counting order) for the inputs & output and you will later compare it with the simulation results.

Boolean Expression

What is the Boolean expression from the logic diagram given below: $Y = (AB') + C'$

Logic Diagram

 

Truth Table

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;  ----- import libraries

entity Lab2 is
port (
    A, B, C : in STD_LOGIC;  ----- port assignments
    Y: out STD_LOGIC
);
end Labex2;

architecture V1 of Lab2 is  ----- logic function
begin
    Y <= (A AND Not B) OR Not C ;

end V1;  ----- end of VHDL code
```

Procedure

The following are the basic steps in implementing a project using Quartus 2. Details for each steps can be found in the handouts provided entitled **Graphical Gate Entry** from Quartus Tutorial.

All design entries can be taken from:

- a) Logic Diagram,
- b) Boolean Expression ,
- c) Truth Table
- d) HDL Code (VHDL or Verilog)

I. Creating a Project in Quartus

- A. New Project Design Creation
Device----Cyclone II --- EP2C35F672C6
- B. Configuring Quartus Window

II. Designing

- A. Creating a Block Diagram/Schematic File (BDF) or VHDL code
- B. Adding Text
- C. Component Selection Process and Moving Components
- D. Adding/Deleting Wires
- E. Adding Input & Output Ports
- F. Compiling
- G. Functional Compiling

III. Simulating

- A. Creating a Vector Waveform File (VWF)
- B. Adding signals
- C. Changing Grid Size and End Time


- D. Manually Changing VWF
- E. Functional and Timing Simulation
- F. Grouping Signals and Using Count Value and Clock Value

IV. Programming (Altera DE2 Board)


- A. Assigning pins using Pin Planner
- B. Tri-stating unused pins
- C. Programming
- E. Exporting Pin Assignments
- F. Deleting Pin Assignments

Outputs:


A	B	C	Y
0	0	0	1

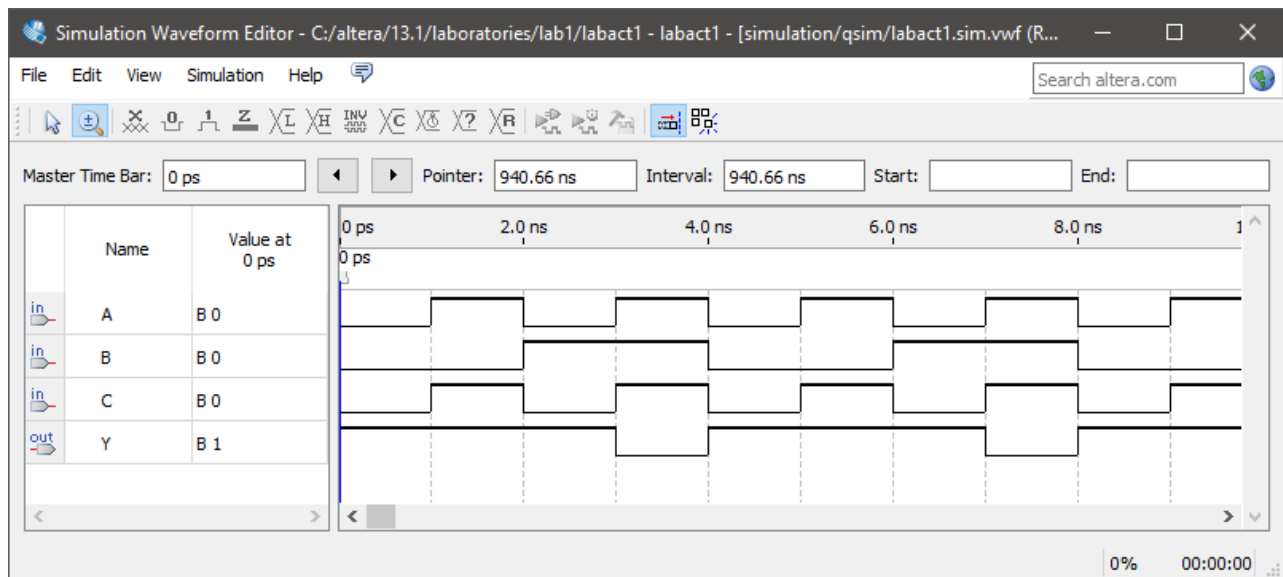


A	B	C	Y
0	0	1	0

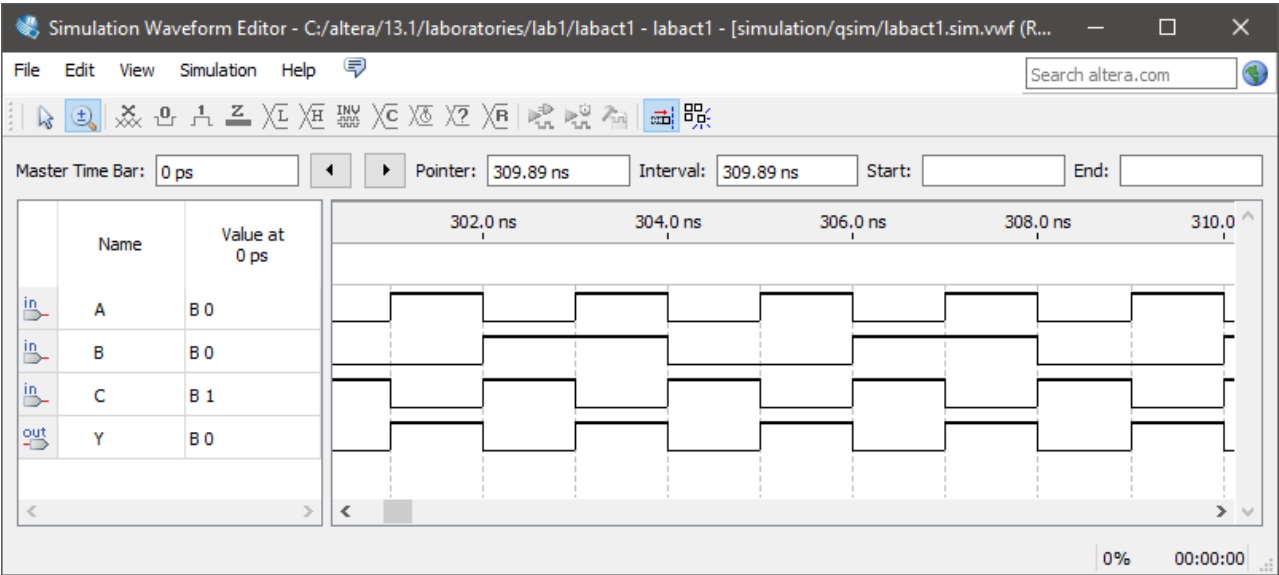


A	B	C	Y
0	1	0	1

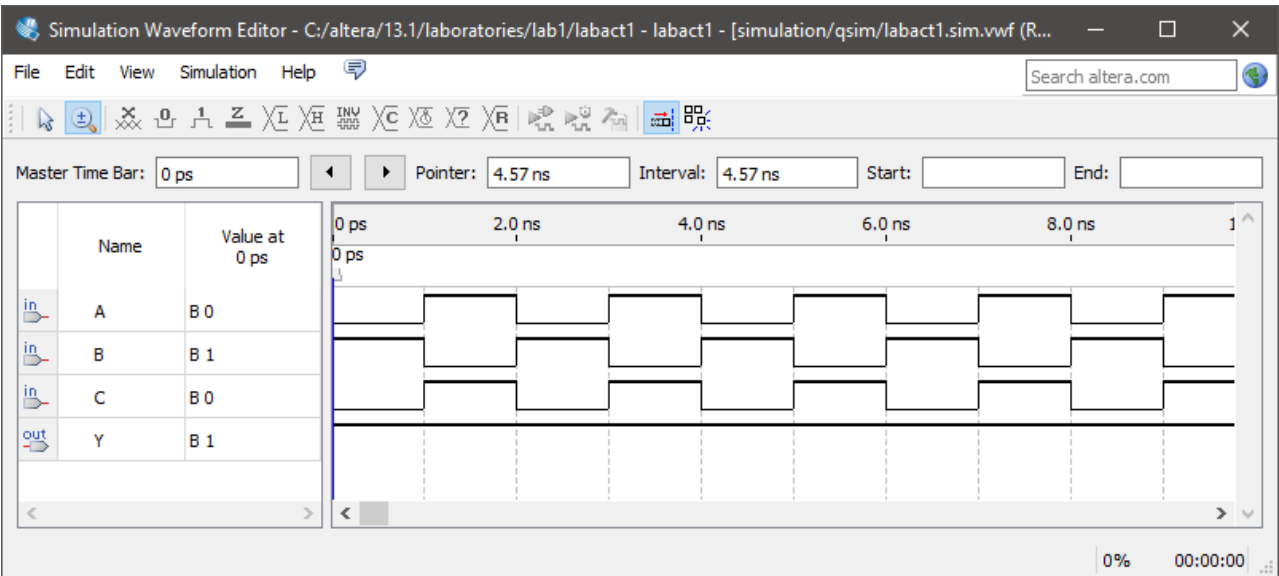


A	B	C	Y
0	1	1	0

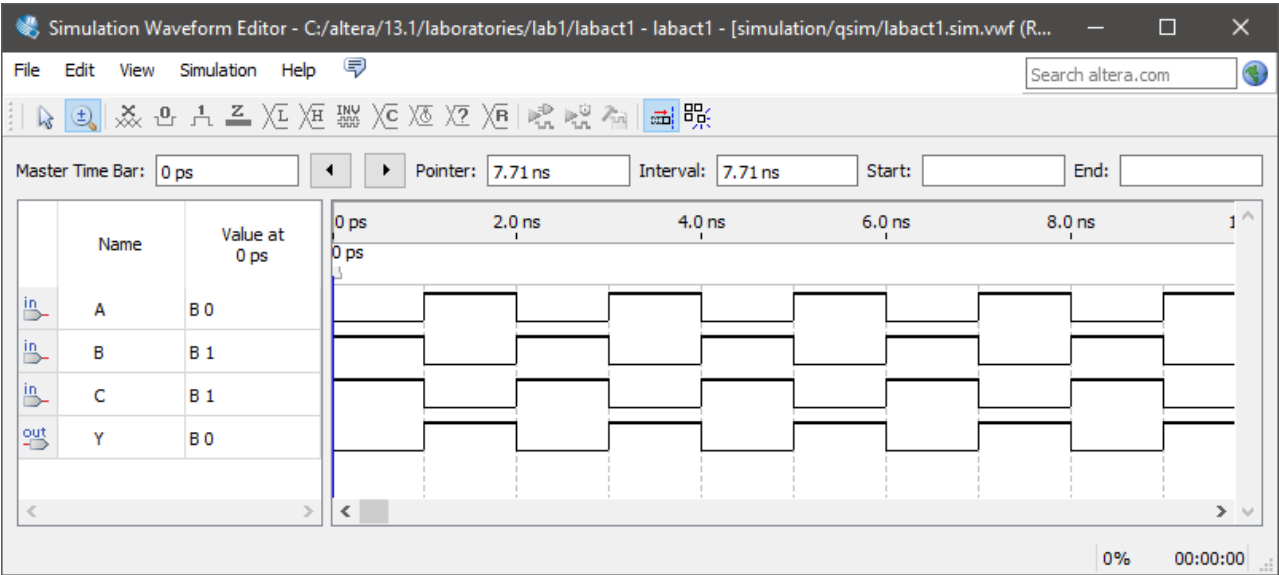


A	B	C	Y
1	0	0	1

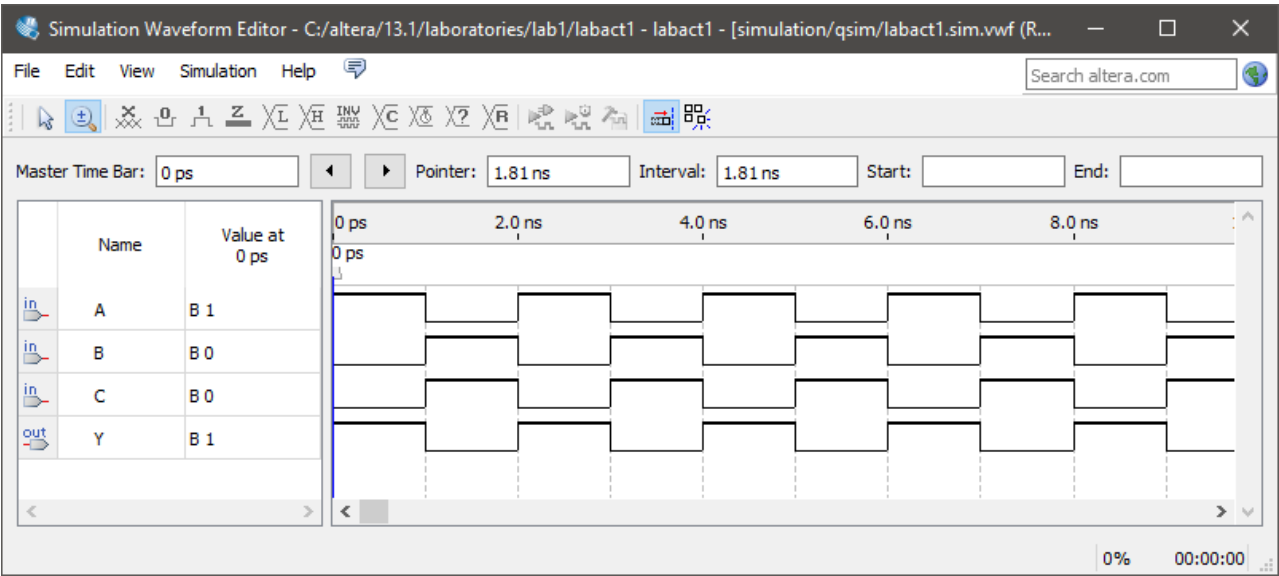

A	B	C	Y
1	0	1	1

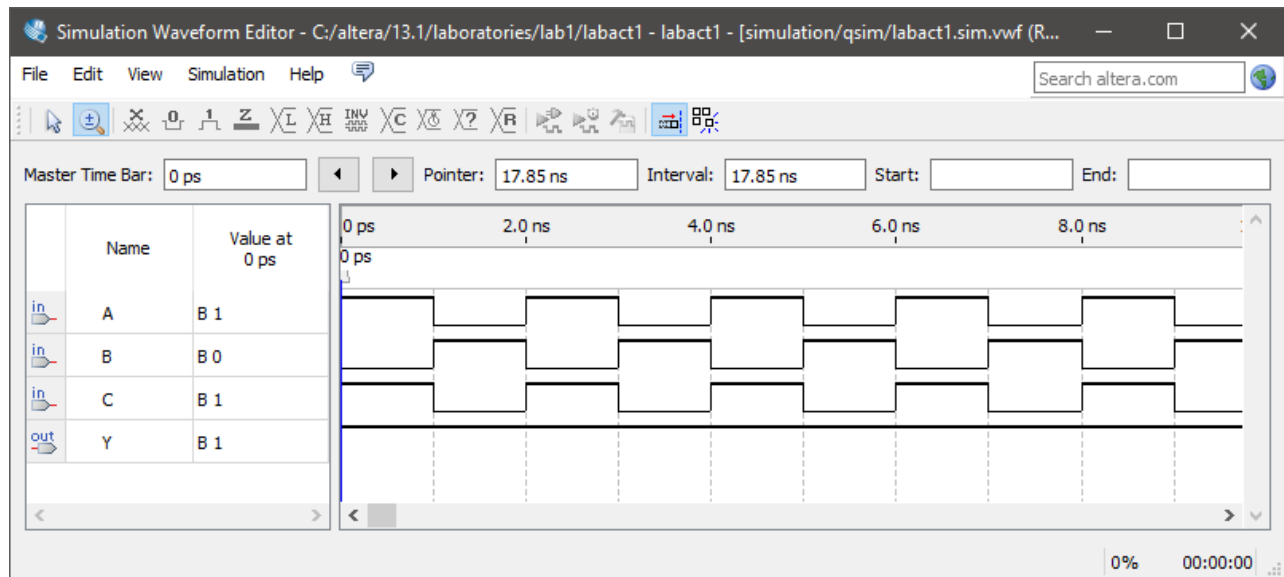

A	B	C	Y
1	1	0	1

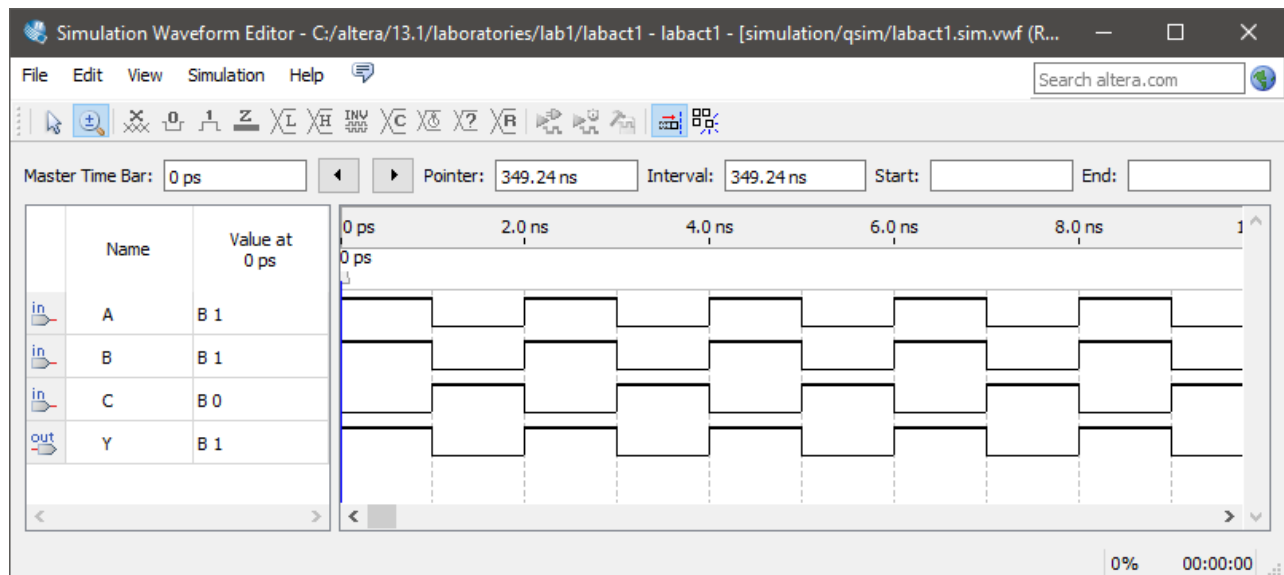

A	B	C	Y
1	1	1	0

